

Problem 1: Design a system for converting process variable $x \in [0, 125 \text{ m}]$, the length of magnetic tape wound on a spool, to a floating-point number $\text{length} = H(x) = x \frac{1}{\text{m}}$. The tape is $15 \mu\text{m}$ thick and does not shrink or stretch; it is wound tightly on the spool so there is no space between the layers of tape. The inner diameter of the spool (without tape) is 5 mm. The radius of the surface layer of tape can be determined by a mechanical contact free to move radially (so its position is linearly related to the surface-layer radius).

The solution should:

- Specify a transducer to convert the position of the mechanical contact to an electrical quantity. You are encouraged to choose the transducer so that the conditioning circuit is as simple as possible.
- Show the mapping between tape length and surface-layer radius.
- Show the mapping between outer radius and transducer response¹.
- Use a 5-volt, 8-bit, analog-to-digital converter.
- Design the conditioning circuit to make full use of the ADC's dynamic range.
- Show the mapping between ADC output and length , H_f .
- Include a schematic showing all component and supply values.
- Include pseudocode for the interface routine; specify values for all constants.

Problem 2: Determine the precision of the value written to length in the problem above.

Problem 3: Design a system for converting process variable $x \in [0, 125 \text{ m}]$, the length of magnetic tape wound on a spool, to a voltage $H(x) = x \frac{10 \text{ V}}{\text{m}}$. The tape and mechanical parts are the same as above. The solution should use only analog components. See footnote for hint².

¹ Since a variable resistor is the only transducer covered, "transducer response" can be replaced with "transducer resistance."

² Hint: Use two variable resistor transducers (measuring the same displacement) and use each in a different inverting amplifier.