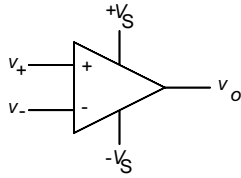


Operational Amplifiers

These are common components in conditioning circuits.

There are two inputs, v_+ and v_- , two power supplies, $+V_s$ and $-V_s$, and an output, v_o .



$$v_o = \min\{+V_s, \max\{-V_s, (v_+ - v_-)A\}\}, \text{ where } A \text{ is the op-amp gain.}$$


Ignoring saturation, $v_o = A(v_+ - v_-)$.

Ideal Op-Amp Properties

Infinite input impedance.

Infinite gain. ($A = \infty$)

Zero output impedance.

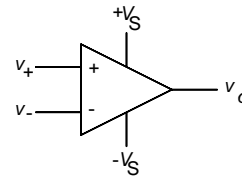

Where to Find Ideal Op-Amps

An electronics textbook.

However, in certain circuits a real op-amp performs almost the same as an ideal op-amp would.

Simplifying Assumptions

Current into inputs is zero.

When used in a negative feedback configuration, $v_+ = v_-$.


Op-Amp Circuits to be Covered

Non-inverting amplifier.

Inverting amplifier.

Summing amplifier.

Non-Inverting Amplifier

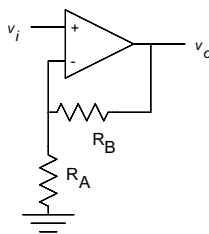

$$v_o = \frac{R_A + R_B}{R_A} v_i.$$

Versatility of Inverting Amplifier


Use of Non-Inverting Amplifier in Conditioning Circuits

$$v_o = \frac{R_A + R_B}{R_A} v_i.$$

Traditional Use, Voltage Amplifier

Input is v_i , output is v_o .

$$H_c(v_i) = \frac{R_A + R_B}{R_A} v_i$$

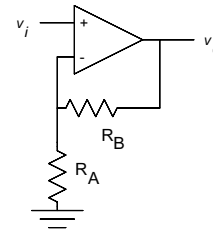

Non-Inverting Amplifier Example Problem

Design a system with output $v_o = H(x)$, where process variable x is water level, $x \in [0 \text{ m}, 1 \text{ m}]$, and $H(x) = 10x \frac{\text{V}}{\text{m}}$.

Note: most example problems will not be as complete as the archetypical problem covered earlier.

Solution:

Use same float-and-cable system as in previous example problem.

Use $100 \text{ k}\Omega$ three-terminal variable resistor with 1 V voltage source across fixed terminals:

$$H_t(x) = 1x \frac{\text{V}}{\text{m}}$$

Problem will be solved two ways:

First way, we know what kind of conditioning circuit is needed.

Second way, we have to determine algebraically the type of conditioning circuit needed.

First Way: Use Non-Inverting Amplifier

Obviously, all that is needed is an amplifier with a gain of 10. A non-inverting amplifier will do.

Then:

$$\begin{aligned} H(x) &= H_c(H_t(x)) = A \left(1x \frac{\text{V}}{\text{m}} \right) \\ 10x \frac{\text{V}}{\text{m}} &= A \left(1x \frac{\text{V}}{\text{m}} \right) \\ A &= 10 \end{aligned}$$

So choose resistors such that $(R_A + R_B)/R_A = 10$.

For example, $R_A = 10 \text{ k}\Omega$ and $R_B = 90 \text{ k}\Omega$.

Second Way: Derive Conditioning-Circuit Function

Pretend we don't know that a simple amplifier is needed.

$$H(x) = H_c(H_t(x))$$

We need to solve for H_c .

$$\text{Let } y = H_t(x) = 1x \frac{\text{V}}{\text{m}}$$

$$\text{Then } x = H_t^{-1}(y) = 1y \frac{\text{m}}{\text{V}}$$

Substituting:


$$\begin{aligned} H \left(1y \frac{\text{m}}{\text{V}} \right) &= H_c(y) \\ H_c(y) &= H \left(1y \frac{\text{m}}{\text{V}} \right) = 10 \left(1y \frac{\text{m}}{\text{V}} \right) \\ &= 10y \end{aligned}$$

Therefore our conditioning circuit needs to multiply y , a voltage, by a constant.


A non-inverting amplifier will do just that.

(The remainder of the solution is identical to the first way.)

Inverting Amplifier

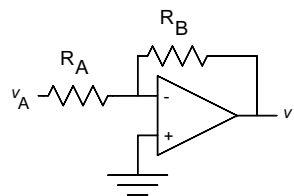

$$v_o = -\frac{R_B}{R_A} v_A$$

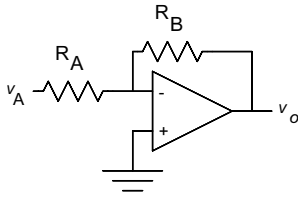

$$\text{Output } v_o = -\frac{R_B}{R_A}v_A.$$

Traditional Use, Voltage Amplifier

Input is v_A and output is v_o .

$$H_c(v_A) = -\frac{R_B}{R_A}v_A = A_1v_A$$

where $A_1 = -\frac{R_B}{R_A}$.


Resistance to Voltage Converter

Input is R_B , output is v_o .

$$H_c(R_B) = -\frac{R_B}{R_A}v_A = A_2R_B$$

where $A_2 = -v_A/R_A$.

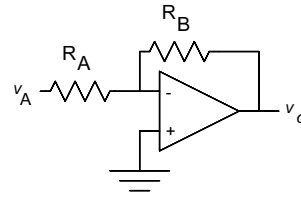Here, v_A is a fixed voltage, buried in the constant A_2 .



Inverted Resistance to Voltage Converter

Input is R_A , output is v_o .


$$H_c(R_A) = -\frac{R_B}{R_A}v_A = A_3/R_A$$

where $A_3 = -R_Bv_A$.

v_A is a fixed voltage here also.

Current to Voltage Converter

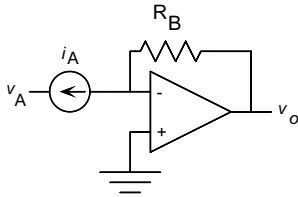This circuit is similar to the inverting amplifier.



Input is i_A , output is v_o .

$$H_c(i_A) = R_Bi_A = A_4i_A.$$

where $A_4 = R_B$.

Inverting Amplifier Example Problem

Design a system with output $v_o = H(x)$, where process variable x is water level, $x \in [0 \text{ m}, 1 \text{ m}]$, and $H(x) = 10x \frac{\text{V}}{\text{m}}$.

This is the same as the non-inverting amplifier problem.

Solution:

Use same float-and-cable system as in previous example problem.

Use a $100 \text{ k}\Omega$ two-terminal variable resistor:

$$H_t(x) = 100x \frac{\text{k}\Omega}{\text{m}}.$$

The variable resistor will be the “input” to the inverting amplifier.

Conditioning-Circuit Function Derivation

So far: $H(x) = 10x \frac{V}{m}$ (given) and $H_t(x) = 100x \frac{k\Omega}{m}$ (choice of transducer).

Solve for H_c in:

$$H_c(H_t(x)) = H(x)$$

$$\text{Let } y = H_t(x) = 100x \frac{k\Omega}{m}.$$

$$\text{Then } x = 0.01y \frac{m}{k\Omega}.$$

Substituting:

$$\begin{aligned} H_c(y) &= H\left(0.01y \frac{m}{k\Omega}\right) \\ &= 10\left(0.01y \frac{m}{k\Omega}\right) \frac{V}{m} \\ &= 0.1y \frac{V}{k\Omega} \end{aligned}$$

For the inverting amplifier used as a resistance-to-voltage converter:

$$H_c(R_B) = A_2 R_B.$$

$$R_B \rightarrow y \text{ and } A_2 \rightarrow 0.1 \frac{V}{k\Omega}.$$


Choose R_A and v_A so that the following equation is satisfied:

$$0.1 \frac{V}{k\Omega} = -\frac{v_A}{R_A}$$

For example, $R_A = 60 k\Omega$ and $v_A = -6 V$.

Another Inverting Amplifier Sample Problem

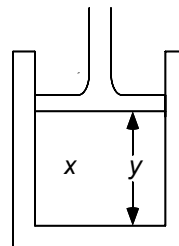Design a system with output $v_o = H(x)$, where process variable x is pressure in a sealed cylinder, $x \in [100 \text{ kPa}, 1000 \text{ kPa}]$, and $H(x) = \frac{x}{100 \text{ kPa}} V$. The cylinder has an area of 100 cm^2 . The piston can reach a maximum height of 10 cm at which point the pressure will be 100 kPa . The cylinder contents is held at a constant temperature.



Plan: Deduce pressure by measuring the position of the piston.

Ideal gas law: $PS = n\mathfrak{R}T$,

where P is the pressure, S is the volume, n is the number of particles, \mathfrak{R} is the universal gas constant, and T is the temperature.

Since the cylinder is sealed, n is constant.

Since a constant temperature is maintained, T is constant.

Then: $PS = n\mathfrak{R}T = 100 \text{ kPa } 10 \text{ cm } 100 \text{ cm}^2 = 10^5 \text{ kPa cm}^3$.

Solution Plan:

Compute position of piston, y , in terms of pressure, x .

Measure position of piston with variable resistor.

Find conversion circuit to produce $H(x)$.

Transducer(s)

Two transducers are being used:

- Pressure-to-position. (The piston.) Use notation $y = H_{t1}(x)$.
- Position-to-resistance. Use notation $z = H_{t2}(y)$.

Pressure to Position

Recall: $PS = 10^5 \text{ kPa cm}^3$.

Here $P \rightarrow x$

...and $S \rightarrow y100 \text{ cm}^2$.

So: $xy100 \text{ cm}^2 = 10^5 \text{ kPa cm}^3$.

$$\text{Or: } y = \frac{10^5 \text{ kPa cm}^3}{x100 \text{ cm}^2} = \frac{10^3 \text{ kPa cm}}{x} = H_{t1}(x).$$

Position to Resistance

Use a $5 k\Omega$ variable resistor.

Connect it such that $H_{t2}(y) = \frac{y}{10 \text{ cm}} 5 k\Omega$.

Conversion Circuit Function

Desired output: $H(x) = \frac{x}{100 \text{ kPa}} V$.

$$H_c(H_{t2}(H_{t1}(x))) = H(x)$$

$$\text{Let } z = H_{t2}(H_{t1}(x)) = 5 \times 10^5 \frac{\text{kPa}}{x} \Omega.$$

$$\text{Then: } x = 5 \times 10^5 \frac{\text{kPa}}{z} \Omega.$$

Substituting:

$$\begin{aligned} H_c(H_{t2}(H_{t1}(x))) &= H(x) \\ H_c(z) &= H\left(5 \times 10^5 \frac{\text{kPa}}{z} \Omega\right) \\ &= \frac{5}{z} k\Omega V \end{aligned}$$

Conversion Circuit Choice

Use inverting amplifier as inverted-resistance-to-voltage converter.


$$H_c(R_A) = \frac{A_3}{R_A}, \text{ where } A_3 = -R_B v_A.$$

$$R_A \rightarrow z \text{ and } A_3 \rightarrow 5 k\Omega V.$$

Choose R_B and v_A so that $5 k\Omega V = -R_B v_A$.

For example, $R_B = 50 k\Omega$ and $v_A = -10 V$

Summing Amplifier

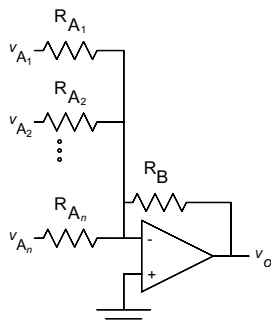

$$v_o = -R_B \sum_{i=1}^n \frac{v_{A_i}}{R_{A_i}}$$

Applications


Adding response of several transducers.

Adding "a constant" to the output of a transducer.

Gain/Offset Circuit


Frequently used conditioning circuit.

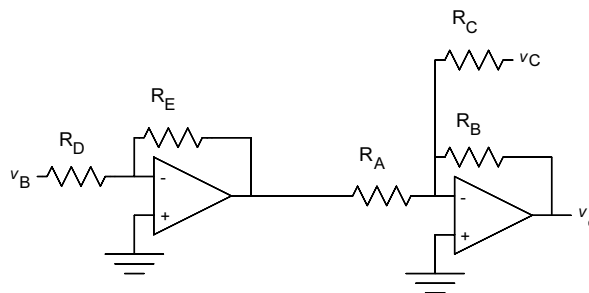Uses one inverting amplifier and one summing amplifier.



$$v_o = \frac{R_B v_B}{R_D R_A} \left(R_E - \frac{v_C R_D R_A}{v_B R_C} \right)$$

Gain/Offset Circuit

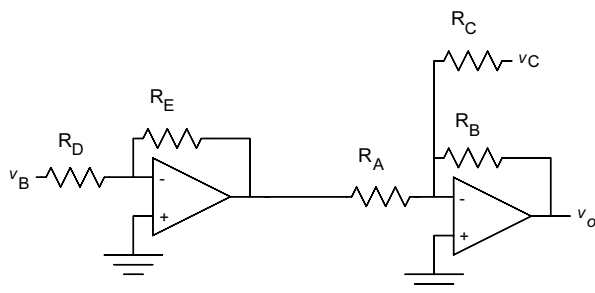

$$v_o = \frac{R_B v_B}{R_D R_A} \left(R_E - \frac{v_C R_D R_A}{v_B R_C} \right)$$

$$v_o = A_5 (R_E - O_5)$$

$$H_c(R_E) = A_5 (R_E - O_5)$$

In this form,

- R_E is the input,
- $A_5 = \frac{R_B v_B}{R_D R_A}$ determines the *gain*,
- and $O_5 = \frac{v_C R_D R_A}{v_B R_C}$ determines the *offset*.

Note that offset can be changed without affecting gain.

Gain/Offset Circuit Example

Design a system with output $v_o = H(x)$, where process variable x is water level, $x \in [0 \text{ m}, 1 \text{ m}]$, and $H(x) = 10x \frac{\text{V}}{\text{m}}$.

This is identical to an earlier problem.

However, it will be solved using a different transducer.

Transducer function will account for the small deviation from perfection.

Transducer:

$$H_t(x) = e_1 \frac{x}{\text{m}} 5 \text{ k}\Omega + e_2,$$

where $e_1 = 0.91$ and $e_2 = 37 \Omega$.

(If $e_1 = 1$ and $e_2 = 0$ then the transducer would be perfect.)

The conditioning circuit should be designed to give the proper output, taking into account e_1 and e_2 .

Proceeding in the usual manner:

$$\text{Let } y = H_1(x) = e_1 \frac{x}{\text{m}} 5 \text{ k}\Omega + e_2.$$

$$\text{Then } x = \frac{\text{m}}{e_1 5 \text{ k}\Omega} (y - e_2).$$

$$\begin{aligned} H_c(H_1(x)) &= H(x) \\ H_c(y) &= 10 \frac{\text{V}}{\text{m}} \frac{\text{m}}{e_1 5 \text{ k}\Omega} (y - e_2) \\ &= \frac{2 \text{ V}}{e_1 \text{ k}\Omega} (y - e_2) \end{aligned}$$

Looks like a gain/offset circuit.

$$A_5 \rightarrow \frac{2 \text{ V}}{e_1 \text{ k}\Omega} \text{ and } O_5 \rightarrow e_2.$$

Choose component values so that following are simultaneously satisfied:

$$\frac{2 \text{ V}}{e_1 \text{ k}\Omega} = \frac{R_B v_B}{R_D R_A} \text{ and } e_2 = \frac{v_C R_D R_A}{v_B R_C}$$

Choose reasonable values for R_A , R_D , v_B , and v_C .

$$v_B = 5 \text{ V and } R_D = 5 \text{ k}\Omega.$$

Possible reasons: a 5 V supply is available.

Current through transducer (R_E) will be 1 mA, not too large or small for many cases.

$$R_A = 10 \text{ k}\Omega \text{ and } v_C = 5 \text{ V}.$$

Solving equations then yields:

$$R_B = 22.0 \text{ k}\Omega.$$

$$R_C = 1.35 \text{ M}\Omega.$$