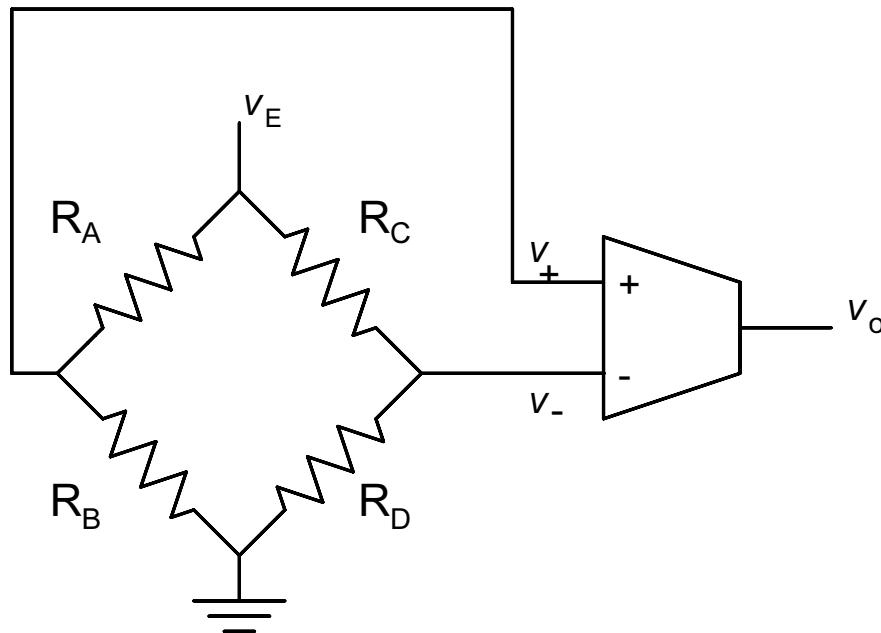


## The Wheatstone Bridge



*Raison d'être:* convert tiny changes in resistance to voltage.

Shown with an *instrumentation amplifier*.


Like an ideal op-amp but with finite gain.

Gain of instrumentation amplifier denoted by  $A$ .

$$v_o = A(v_+ - v_-).$$

The Wheatstone bridge consists of four *arms*.
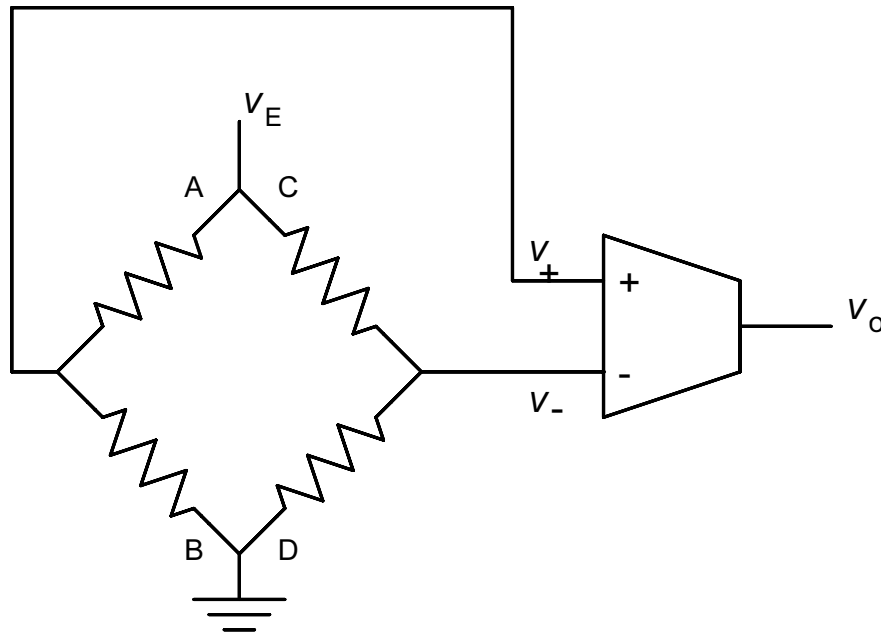
$$v_o = A \left( \frac{R_B}{R_A + R_B} - \frac{R_D}{R_C + R_D} \right) v_E.$$



Transducer can be placed in one, two, or four arms.

Typical function:  $H_t(x) = R(1 + xk)$ ,  $xk \ll 1$

where  $R$  is the nominal resistance of the transducer and  $k$  is a constant.

For simplicity write function as:  $H_t(x) = R + R_s$ ,

where  $R$  is independent of the process-variable value and  $R_s$  is dependent on the process-variable value.

Typically,  $R \gg R_s$ .

Usually, need to convert  $R_s$  to a voltage.

## Complementary Pairs

Frequently, transducer pairs can have *complementary responses*.

If so, there are two (usually identical) transducers...

...positioned so they react *oppositely* to the process variable...

...so that when their responses are *subtracted*...

...their response to the process variable *add*...

...and unwanted quantities *cancel out*.


For example, consider:

$$H_{t1}(x) = R(1 + xk) \text{ and } H_{t2}(x) = R(1 - xk).$$

Sum:  $H_{t1}(x) + H_{t2}(x) = R$ . (Not helpful.)

Difference:  $H_{t1}(x) - H_{t2}(x) = 2xk$ . (Much better.)

## One-Transducer Configuration

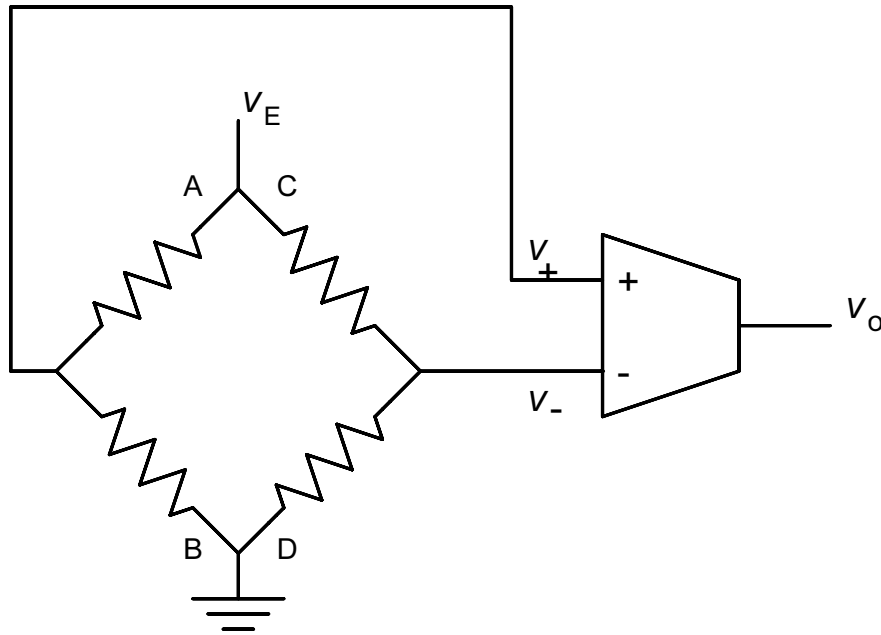


Arm B:  $H_t(x) = R + R_s = R(1 + xk)$ .

Other Arms: Resistor of value  $R$ .

$$v_o = A \left( \frac{R_s}{2(2R + R_s)} \right) v_E \approx A \frac{R_s}{4R} v_E = A \frac{xk}{4} v_E.$$

## Two-Transducer Configuration

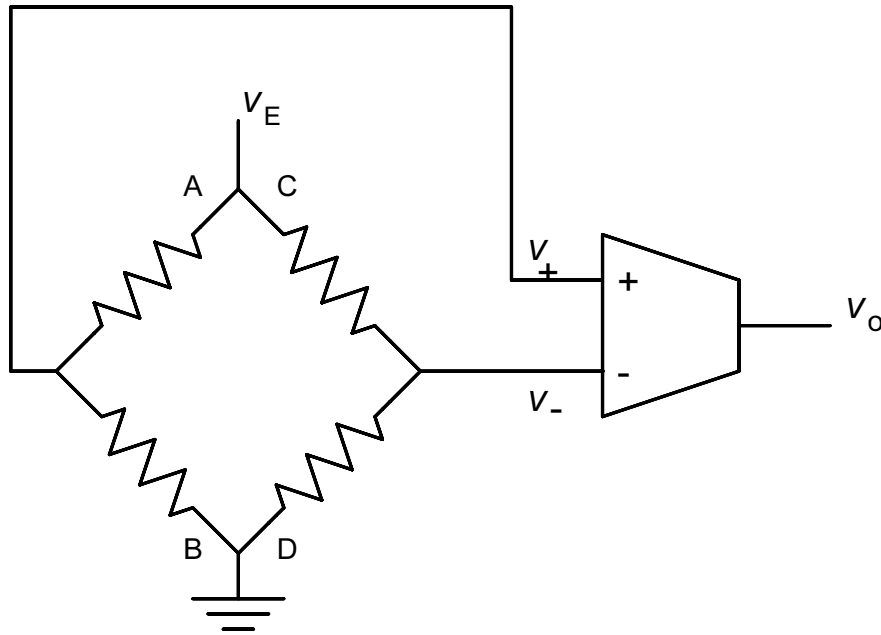

Arm A:  $H_{t2}(x) = R - R_s = R(1 - xk)$ .


Arm B:  $H_{t1}(x) = R + R_s = R(1 + xk)$ .

Other Arms: Resistor of value  $R$ .

$$v_o = A \frac{R_s}{2R} v_E = A \frac{xk}{2} v_E.$$

As one might expect, twice as sensitive.

## Four-Transducer Configuration

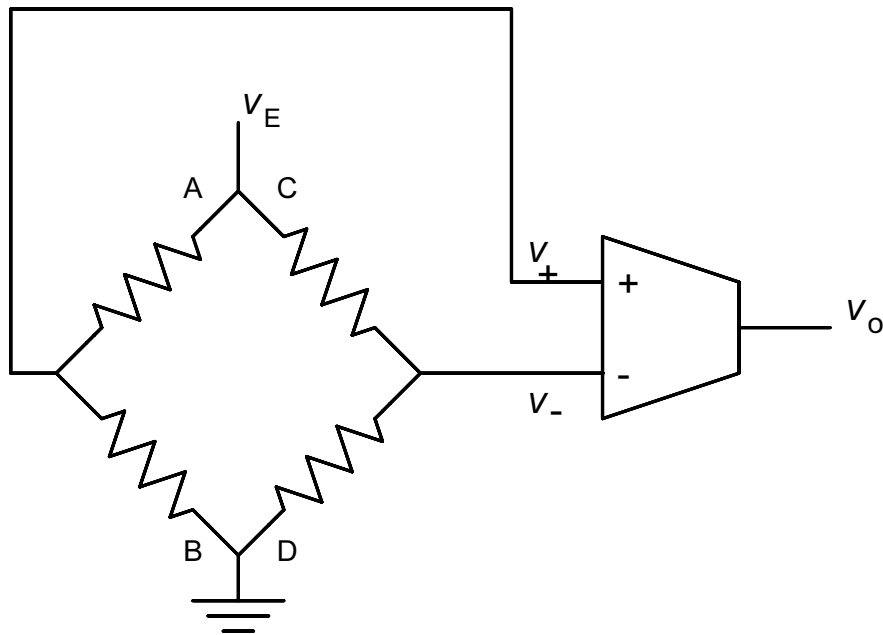

Arms A and D:  $H_{t2}(x) = R - R_s = R(1 - xk)$ .

Arms B and C:  $H_{t1}(x) = R + R_s = R(1 + xk)$ .

$$v_o = A \frac{R_s}{R} v_E = Axkv_E.$$

## Wheatstone Bridge Transfer Functions

### Goal

Let  $R_t = R \pm R_s = R(1 \pm xk)$  be the transducer response(s).

Assume bridge designed properly.

Need to find two functions:

$$H_c(R_t) = \dots \quad \text{and} \quad H_c(R_s) = \dots$$

Both functions are equivalent.

Choose whichever is more convenient.

### Four-Transducer Configuration

$$H_c(R_s) = v_o = A \frac{R_s}{R} v_E.$$

Let  $R_t = R + R_s$ . Then  $R_s = R_t - R$ .

$$H_c(R_t) = A \frac{R_t - R}{R} v_E = A \left( \frac{R_t}{R} - 1 \right) v_E.$$

### Two-Transducer Configuration

$$H_c(R_s) = v_o = \frac{A}{2} \frac{R_s}{R} v_E.$$

$$H_c(R_t) = \frac{A}{2} \frac{R_t - R}{R} v_E = \frac{A}{2} \left( \frac{R_t}{R} - 1 \right) v_E.$$

### One-Transducer Configuration

$$H_c(R_s) = v_o = \frac{A}{4} \frac{R_s}{R} v_E.$$

$$H_c(R_t) = \frac{A}{4} \frac{R_t - R}{R} v_E = \frac{A}{4} \left( \frac{R_t}{R} - 1 \right) v_E.$$

## Wheatstone Bridge Sample Problem

*Design a system with output  $v_o = H(x)$ , where process variable  $x$  is strain and,  $x \in [0, 10^{-5}]$ , and  $H(x) = 10^6 x$  V.*

Strain will be covered in more detail later.

For now, all we need to know is that strain is dimensionless.

Strain is measured by a *strain gauge*.

Strain gauges frequently used in complementary pairs.

Use strain gauges with response:

$$H_t(\epsilon) = R(1 + \epsilon G_f),$$

where  $\epsilon$  denotes strain and

constant  $G_f = 2$ .

( $G_f$  called *gauge factor*, a dimensionless quantity.)

Position the two strain gauges to obtain response:

$$H_t(x) = R(1 + xG_f) \quad \text{and} \quad H_{t'}(x) = R(1 - xG_f).$$



## Derivation of Conditioning Circuit Needed

A Wheatstone bridge is the obvious choice because transducer response is in form  $R \pm R_s$ .

Nevertheless, conditioning-circuit derivation will be presented.

$$H(x) = H_c(H_t(x))$$

(Analysis performed as though there were one transducer.)

$$y = H_t(x) = R_t = R(1 + xG_f). \text{ Then } x = \frac{\frac{y}{R} - 1}{G_f}.$$

$$\text{Then } H_c(y) = H\left(\frac{\frac{y}{R} - 1}{G_f}\right) = 10^6 \frac{\frac{y}{R} - 1}{G_f} \text{ V.}$$

$$\text{Response for two-transducer configuration: } H_c(R_t) = \frac{A}{2} \left( \frac{R_t}{R} - 1 \right) v_E.$$

Choose  $A$  and  $v_E$  so that  $\frac{A}{2} v_E = \frac{10^6}{G_f} \text{ V}$  is satisfied.

For example,  $v_E = 10 \text{ V}$  and  $A = 10^5$ .