

EE 4770

Homework I

Due: 1 February 1993

**Problem 1:** The water level in a tank is to be measured using a variable resistor. Design a conversion circuit with an output  $v_o = \frac{x}{100 \text{ mm}} \text{ V}$ , where  $x$  is the water level. The output should be 0.00 volts when the tank is empty and 10.0 V when the tank is full. The variable resistor will read 47.0 k $\Omega$  when the tank is empty and 1.00 k $\Omega$  when the tank is full. (The variable resistor cannot be changed.)

**Problem 2:** Design an op-amp threshold detector with  $v_{\text{th-low}} = 5.00 \text{ V}$  and  $v_{\text{th-high}} = 6.00 \text{ V}$ .

EE 4770

Homework II

Due: 15 February 1993

**Problem 1:** A system is to measure the temperature difference between two sides of a barrier. The system is to use a wheatstone bridge, an instrumentation amplifier, and four thermistors. Each thermistor has  $\beta = 3200 \text{ K}$  and  $R_A = 0.0500 \Omega$ . The bridge excitation voltage [denoted  $v_E$  in RTS '95] is to be 15 V. In the schematic diagram show the location of each thermistor with respect to the barrier. Call the output of the circuit  $v_o$  and the temperature difference  $\Delta T$ . For what instrumentation amplifier gain will  $v_o = 10.0 \Delta T \frac{\text{V}}{\text{K}}$  at  $T \approx 250 \text{ K}$  and  $\Delta T \in [-1.00, 1.00]$ ?

EE 4770

Homework III

Due: 5 March 1993

**Problem 1:** A Type-R thermocouple is at a temperature of 1506°C. It is connected to copper wires with an isothermal block. The copper wires are connected to a voltmeter which reads 17.412 mV. What is the temperature of the isothermal block?

**Problem 2:** Find a 60-Watt light bulb package. Assuming the bulb irradiates uniformly in all directions find the illuminance on a point at 2 meters from the bulb. Why was the first assumption made? Does the first assumption help in finding the luminous intensity?

**Problem 3:** Estimate  $K_s$  for the CLT 4140 phototransistor using the attached manufacturer's datasheet.

EE 4770

Homework IV

Due: 14 April 1993

**Problem 1:** Design a circuit to convert temperature to a digital quantity. Temperature in the range of 300 to 301 K should be measured so that  $N = (T - 300 \text{ K})255/\text{K}$ , where  $N$  is the circuit output. The circuit should be based on a single ramp analog to digital converter, *with one of the components replaced by a thermistor*. In order to obtain the proper output the counter circuit as used in a typical single ramp converter cannot be used; make the appropriate modifications. Do not use any arithmetic components (*e.g.*, adders) in your design. Specify values for all components and supplies. Use a thermistor with  $R_A = 0.05 \Omega$  and  $\beta = 3200$ , and a precision supply of  $v_r = 5.00 \text{ V}$ .

**Problem 2:** Design a three-step 12 bit analog to digital converter (similar to the two-step converter described in class). The converter should convert voltages in the range of 0 to 20 V.